



정보통신 수학 및 실습 Homework



학번 : 2016110056


학과 : 불교학부

이름 : 박승원

날짜 : 2017년 5월 1일

Chapter 8 Homework

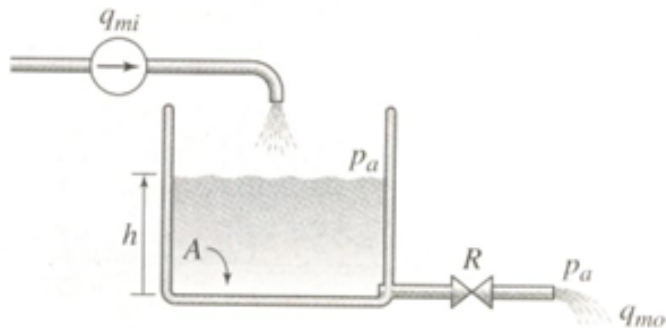1. If the outlet is a pipe that discharges to atmospheric pressure p_a and provides a resistance, R , to flow that is proportional to the pressure difference across its ends, then find the outlet flow rate q_{mo} and the differential equation of $h(t)$.
Hint: q_{mo} is $(1/R)^*$ (the pressure difference across its ends)



A hydraulic system with a flow source.

$$\frac{dm}{dt} = \rho A \frac{dh}{dt} = q_{mi} - q_{mo}$$

$$q_{mo} = q_{mi} - \rho A \frac{dh}{dt} = \frac{1}{R} P = \frac{\rho h(t)}{R}$$

$$q_{mi} - \rho A \frac{dh(t)}{dt} = \frac{\rho h(t)}{R}$$

$$\frac{1}{A} \left(\frac{q_{mi}}{\rho} - \frac{h(t)}{R} \right) = \frac{dh(t)}{dt} = \frac{h(t + \Delta t) - h(t)}{\Delta t}$$

$$h(t + \Delta t) = \frac{\Delta t}{A} \left(\frac{q_{mi}}{\rho} - \frac{h(t)}{R} \right) + h(t)$$

$$h(k + 1) = \frac{\Delta t}{A} \left(\frac{q_{mi}}{\rho} - \frac{h(k)}{R} \right) + h(k)$$

2. Find a DE for the following circuits.

a)

$$Q = CV$$


$$V = \frac{Q}{C}$$

$$V(t) = \frac{1}{C} \int_{t_0}^t I(t) + V(t_0)$$

$$\therefore Q = \int_{t_0}^t I(t)$$

$$V = L \frac{dI(t)}{dt}$$

$$C \frac{dV(t)}{dt} = I(t)$$

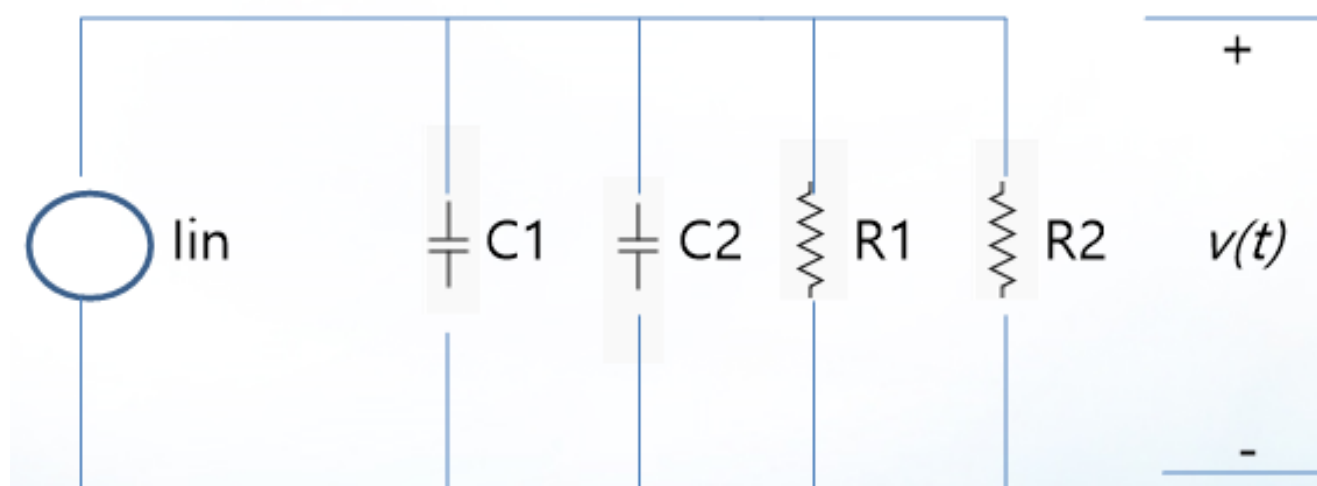

b)

